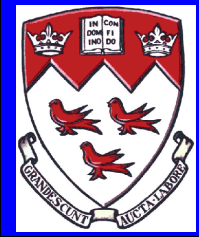




COMP 273

Digital Logic (Part 4) Designing Gateway Networks


Prof. Joseph Vybihal





Announcements

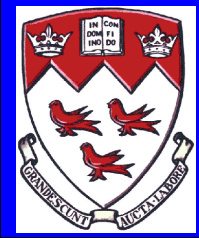- Note: these slides cross over two lectures.





Readings

* Web Resource:

- <http://www.play-hookey.com/digital/>
- http://en.wikipedia.org/wiki/Flip-flop_%28electronics%29

* Appendix C1 to C11 from our textbook



At Home

- Go through the Flip-Flop, Counter and ALU circuit diagrams to understand how they function
- Go on the web and look for the 6502 circuit CPU diagram and try to understand it. This is a classic simple CPU.
- Soul Of A New Machine




Try This Out At Home

- Create a circuit diagram for a candy dispenser machine. You type in a code number and one candy falls out.
 - Think about input of money
 - Returning change
 - Canceling the transaction



Lecture Outline

- Flip-flops & memory
- Designing circuit networks
- Combinatorial logic

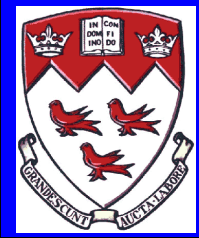




Part 1

The Bit, RAM, Counters, Clocks and Adders




Basic Logic Circuits

Means inverts

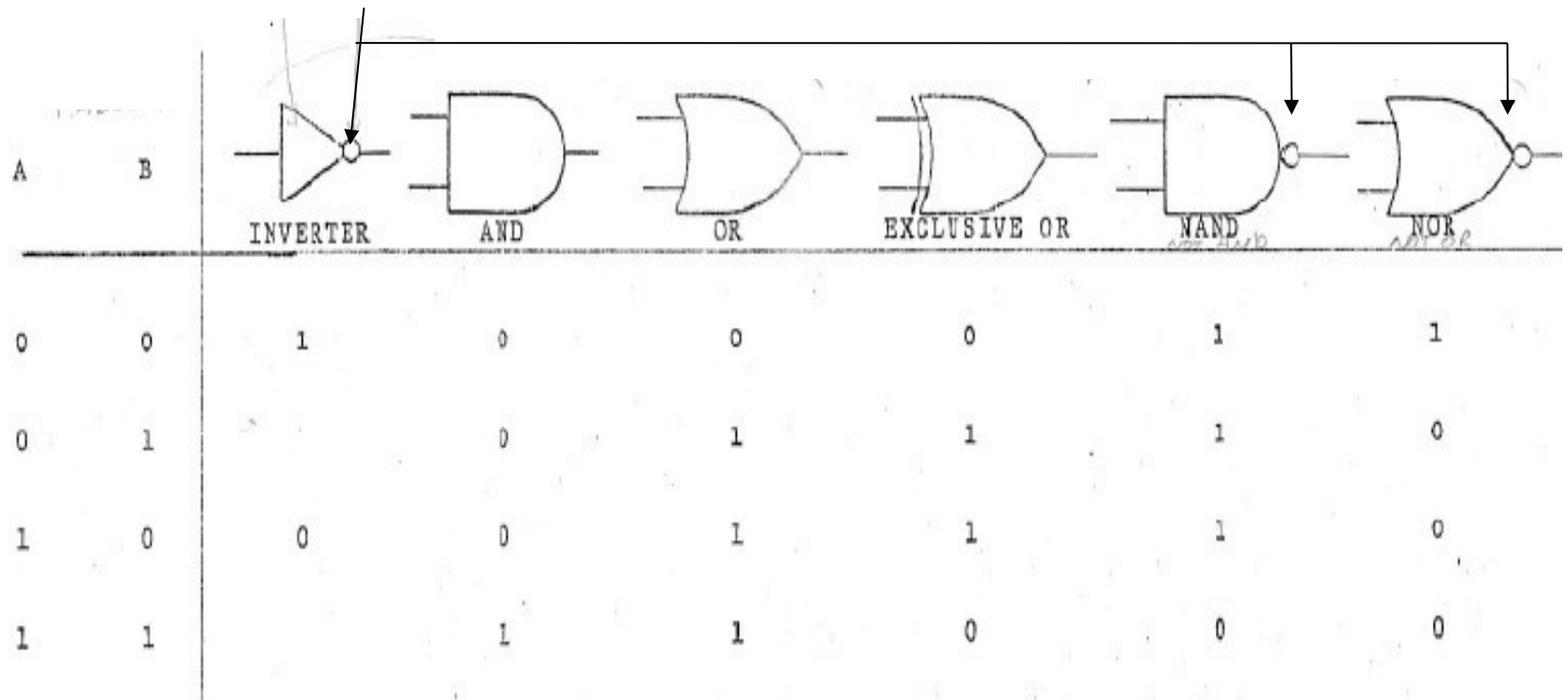

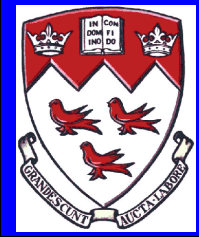
Uni-directional (in this case left to right)





RS Flip Flop

Signal stabilization wait

 


Where is the bit saved?



The Mechanics of Saving

$R \ \& \ S = 0$ then Nothing changes

 

Similar clocked mechanism on this side.


Clocked RS Flip Flop



 Example



What does the circuit of a full 2-byte read/write memory look like?

Hint: Flip-flops and incremental development







Basic Flip Flop Circuits

  




Basic Flip Flop Circuits

 
 


 Arbitrary JPL engineer assignment of letters: J mean set and K mean reset;
 J=1,K=0 SET; J=0,K=1 RESET; J=1,K=1 TOGGLE; J=0,K=0 NOTHING.





Binary Counter


 
 




Basic Adder

HALF-ADDER


2 bits in, Sum, Carry out

   




Basic Adder (Half-Adder)

Without XOR

 


Nicer

 




Full Adder

FULL ADDER 3 bits in, Sum, Carry out

 


Use two half adders and an OR circuit

 



Full Adder

Faster execution

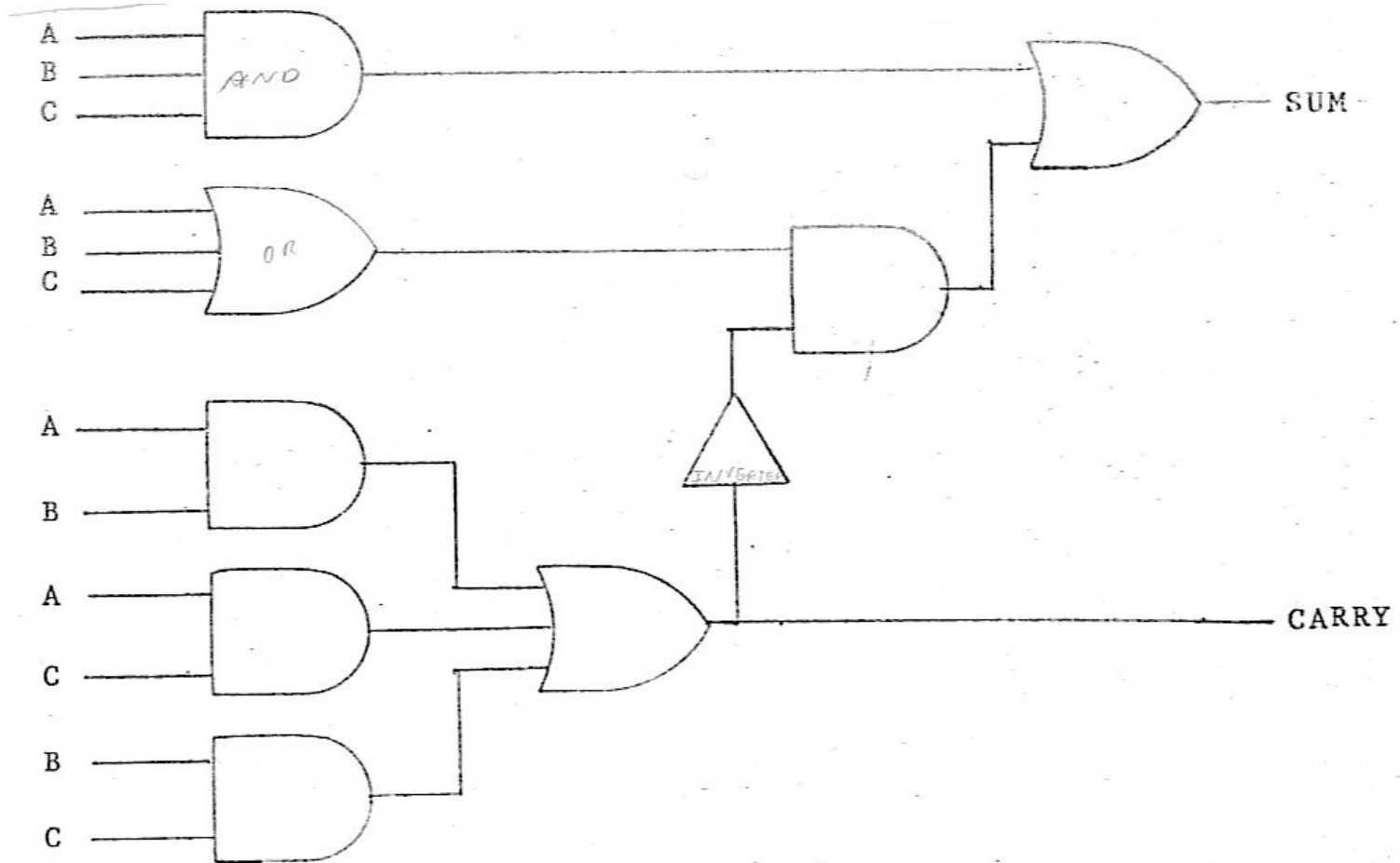



An ALU

TTL
MSI

TYPE SN74S381
ARITHMETIC LOGIC UNIT/FUNCTION GENERATOR

BULLETIN NO. DLS 7412124, MARCH 1974


PIN DESIGNATIONS

DESIGNATION	PIN NOS.	FUNCTION
A3, A2, A1, A0	17, 19, 1, 3	WORD A INPUTS
B3, B2, B1, B0	16, 18, 2, 4	WORD B INPUTS
S2, S1, S0	7, 6, 5	FUNCTION-SELECT INPUTS
C _n	15	CARRY INPUT FOR ADDITION, INVERTED CARRY INPUT FOR SUBTRACTION
F3, F2, F1, F0	12, 11, 9, 8	FUNCTION OUTPUTS
P	14	INVERTED CARRY PROPAGATE OUTPUT
G	13	INVERTED CARRY GENERATE OUTPUT
V _{CC}	20	SUPPLY VOLTAGE
GND	10	GROUND

- A Fully Parallel 4-Bit ALU in 20-Pin Package for 0.300-Inch Row Spacing
- Ideally Suited for High-Density Economical Processors
- Parallel Inputs and Outputs and Full Look-Ahead Provide System Flexibility
- Arithmetic and Logic Operations Selected Specifically to Simplify System Implementation:
 - A Minus B
 - B Minus A
 - A Plus B
 - and Five Other Functions
- Schottky-Clamped for High Performance
 - 16-Bit Add Time . . . 29 ns Typ Using Look-Ahead
 - 32-Bit Add Time . . . 34 ns Typ Using Look-Ahead

description

The SN74S381 is a Schottky TTL arithmetic logic unit (ALU)/function generator that performs eight binary arithmetic/logic operations on two 4-bit words as shown in the function table. These operations are selected by the three function-select lines (S0, S1, S2). A full carry look-ahead circuit is provided for fast, simultaneous carry generation by means of two cascade outputs (P and G) for the four bits in the package. The method of cascading SN54182/SN74182 or SN54S182/SN74S182 look-ahead carry generators with these ALU's to provide multi-level full carry look-ahead is illustrated under typical applications data for the '182 and 'S182. The typical addition times shown above illustrate the short delay time required for addition of longer words when full look-ahead is employed. The exclusive-OR, AND, or OR function of two Boolean variables is provided without the use of external circuitry. Also, the outputs can be either cleared (low) or preset (high) as desired.

 


FUNCTION TABLE

SELECTION	ARITHMETIC/LOGIC
S2 S1 S0	OPERATION
L L L	CLEAR
L L H	B MINUS A
L H L	A MINUS B
L H H	A PLUS B
H L L	A ⊕ B
H L H	A + B
H H L	AB
H H H	PRESET

H = high level, L = low level

ARITHMETIC LOGIC UNIT

 functional block diagram and schematics of inputs and outputs






ALU Questions

- What do we need to assume about our data to build an ALU?
- How would the assumptions impact the design of the ALU?
- In general, how would a 4-bit integer ALU that does addition and subtraction look like? What do you think it would need?
- How would the ALU design change when upgrading a 4-bit integer adding and subtracting ALU to an 8-bit version?



General Circuit Questions

 - Construct a circuit that implements a truth table
- Construct a simple 3 bit increment by 1 circuit (do not use adder)
- 2's complement circuit?
- Construct a circuit that picks 1 bit out of an 2-bit bus given a 1-bit positive binary integer number
 - What about 4-bit bus & 2-bit binary number



Designing gateway networks

EXAMPLE

Binary Code Decimal Example

Example 1.2: BCD-to-seven-segment decoder Figure 1.7 shows how the decimal digits 0–9 might appear on a seven-segment display device. Design logic circuits to generate the enable signals that cause the segments to be lit or darkened, given a 4-bit binary representation of the decimal digit (binary-coded decimal or BCD code) to be displayed as input.



Figure 1.7 Seven-segment display of decimal digits. The three open segments may be optionally used. The digit 1 can be displayed in two ways, with the more common right-side version shown.





Working Truth Table

DIGIT INPUT:

abcd

0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001



OUTPUT:

0123456

1111110



0110000


etc

  




Now Construct the Circuit

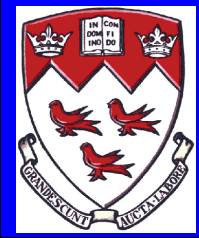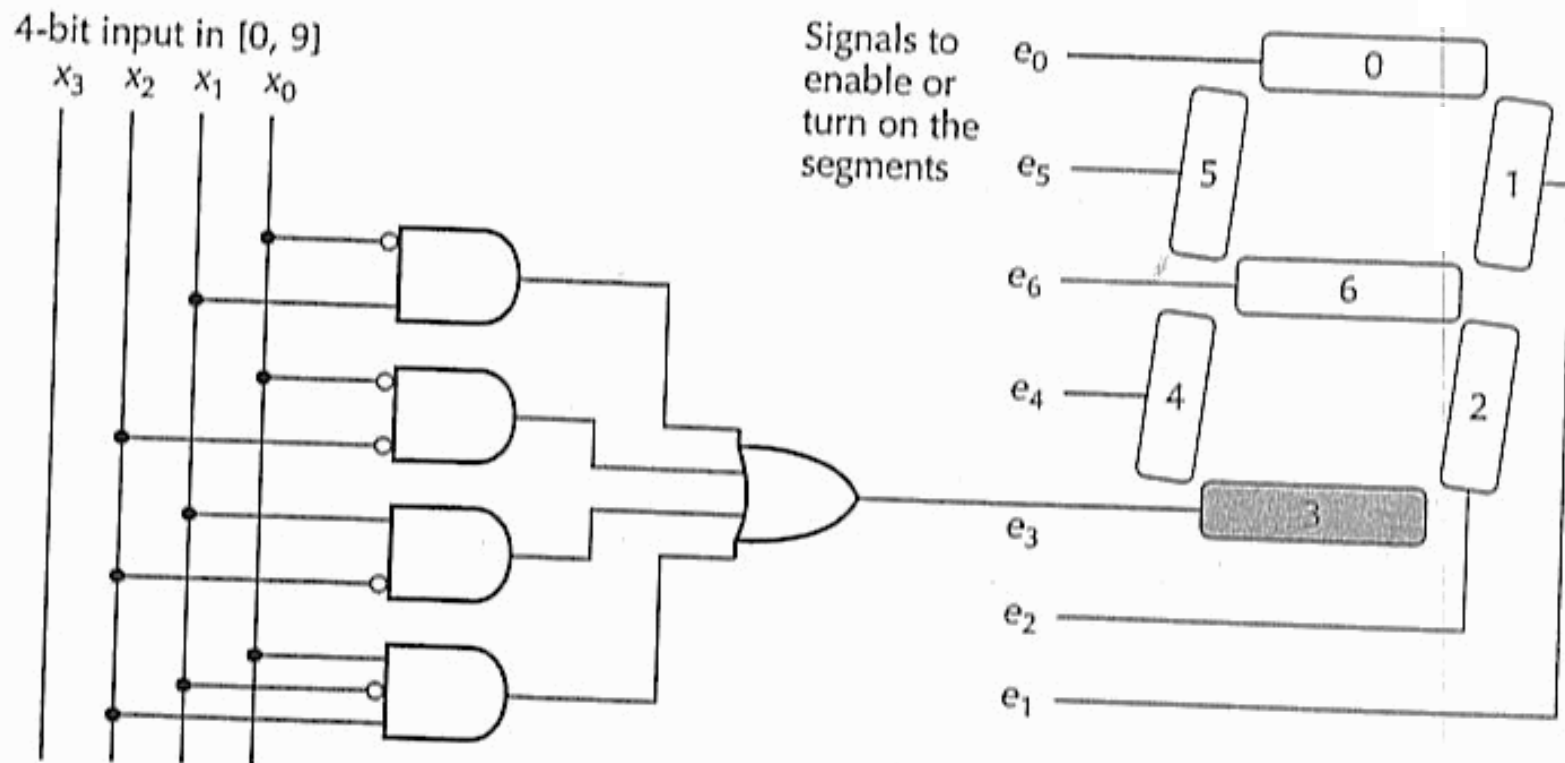

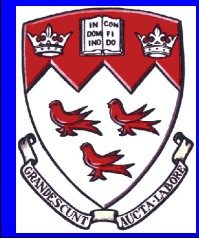

 
Part 2

Useful (off-the-shelf) Combinatorial Networks




Multiplexers

 
Definition: 2^a -to-1 mux has 2^a inputs x_0, \dots, x_{n-1} and a single output z . A selector address 'a' composed of input signals y_0, \dots, y_{a-1} selects which x_i signal passes through z .



Switch View

 

Symbolic View

 


Circuit View

Multiplexers and networks?




Decoders

 Definition: a-to- 2^a decoder asserts one and only one of its 2^a output lines.



2-4 Decoder

Binary number triggers
1 output line


 


Turn on a switch...
The CPU Sequencer...



Encoders

  Definition: Outputs an a -bit binary number, y_i , equal to the index of the single 1 signal among its 2^a inputs, $x_0 \dots x_{a-1}$.




Active is used to tell us if x_0 is ON as compared with circuit turned off.

Hardware error codes...

Programmable Combinatorial Parts (PLA, PROM, ROM)

Type 1: VIA fuses that can be “blown” given sufficient current.

 Type 2: VIA anti-fuse that “set” given sufficient current.





Note






ROM & PROM

  

Fuses not blown

 

Fuses are set, not yet so in this example. Suggestions?





PLA & PAL

 


Figure 1.13 Programmable combinational logic: general structure and two classes known as PAL and PLA devices. Not shown is PROM with fixed AND array (a decoder) and programmable OR array.

PAL = Programmable Array Logic


PLA = Programmable Logic Array



PLA Question

Given a 2 bit binary number, use a PLA that sends out a single bit signal for each binary value: 00, 01, 10, 11.

(Like a decoder)

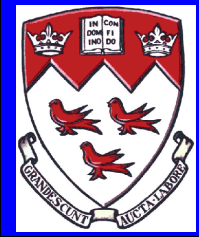



More Questions...

- Assume a temperature is stored in a register as a binary number, assume an alarm is on when it receives an input signal. Set the alarm when the temperature is at or above 500.
- Numeric key-pad operation with num-lock feature (home, up, pg-up, left, nothing, right, end, down, pg-dn, ins, del, / * - + and enter).
- Robot obstacle avoidance circuit: motor on/off, left on/off, right on/off, forward sensor, left sensor, and right sensor. Write a circuit that will cause the robot to follow the wall on its left.
 - What do we need? (equipment, input, output)